



Components List

Designation	Qty	Value& P/N	Description	Vendor
R1	1	27Ω_1%	Current Sense Resistor	Std
R2	1	120KΩ_1%	Feedback Resistor (recommend)	
R3	1	240KΩ_1%	PWM Dimming Control Bias Resistor	
R4	1	620KΩ_1%	PWM Dimming Control Mixer Resistor	
C1	1	4.7μF	Input Capacitor	TAIYO YUDEN
C2	1	0.1μF	Output Capacitor	
C3	1	1μF	Input Capacitor	
C4	1	1μF	Output Capacitor	
C5	1	0.1μF	Bypass Capacitor	
L1	1	10μH/0.5A IDC (LQH32CN100K31)	Inductor	MURATA
		10μH/0.5A IDC (976AS-100M)	Inductor	TOKO
D1	1	0.5A/30V(MBR0530)	Schottky Diode	ON Semi
U1	1	G5103	Micro Power Step-up DC/DC Converter	Global Mixed-Mode Technology
U2	1	G914C	Mirco power LDO regulator. V _{OUT} =3.0V	http://www.gmt.com.tw
U3	1	PIC12C509A	8 bits micro-controller	Miicrochip
SW1~3	3		Push button switch	Std
LED1~4	4	NSCW100	White LED	NICHIA corporation

Circuit Description

The demo board is configured as a constant current supply. Current regulation is accomplished by regulating the voltage across a current sense resistor R1. For dimming the LEDs is to inject a pulse width modulated (PWM) voltage for analog dimming. With this method, the PWM control voltage is converted to its equivalent analog control voltage. The demo board is designed so that the negative duty cycle from 0% to 100% varies the LED current from 0mA to 20mA. The output current increases as the duty cycle increases. Use the equation below to calculate the correctly resistor values.

V_{BAT}: Li-Ion battery power input, bypass to ground with a 4.7μF MLCC capacitor.

V_{BIAS}: +3.0VDC provide a PWM dimming DC bias voltage. It is generated by G914C from V_{BAT}.

R1: is LED current sense resistor. $R1 = 0.60V / I_{LED,MAX} = 0.60V / 20mA = 30\Omega$

R2: is feedback resistor, 120KΩ is recommended.

R4: is PWM dimming control mixer resistor. The value is depended on PWM dimming control signal amplitude. $R4 = (V_H - V_L) / (0.6V / 120K\Omega)$. (maximum value, a little small value could be used)

For 3.0V PWM control signal: $R4 = 3V / (0.6V / 120K\Omega) = 600K\Omega$.

For 3.3V PWM control signal: $R4 = 3.3V / (0.6V / 120K\Omega) = 660K\Omega$.

For 5.0V PWM control signal: $R4 = 5V / (0.6V / 120K\Omega) = 1M\Omega$.

R3: is PWM dimming control bias resistor. The value is depended on V_{BIAS} voltage.

$R3 = (V_{BIAS} - V_{FB}) / [(0.6V/120 K\Omega) + (V_{FB} / R4)]$.

For 3VDC V_{BIAS}: $= (3.0V - 1.2V) / [(0.6V/120 K\Omega) + (1.2V / 600 K\Omega)] = 257 K\Omega$.

For 3.3VDC V_{BIAS}: $= (3.3V - 1.2V) / [(0.6V/120 K\Omega) + (1.2V / 660 K\Omega)] = 308 K\Omega$

For 5VDC V_{BIAS}: $= (5.0V - 1.2V) / [(0.6V/120 K\Omega) + (1.2V / 1000 K\Omega)] = 612 K\Omega$

After choose suitable resistors, designer should check I_{LED} again.

When PWM dimming signal is low (almost equal to 0V):

$$I_{LED} = V_{R1} / R1$$

$$V_{R1} = V_{FB} - V_{R2}$$

$$V_{R2} = I_{R2} \times R2$$

$$I_{R2} = I_{R3} - I_{R4} - I_{FB} = (V_{R3} / R3) - (V_{R4} / R4) - I_{FB} = ((V_{BIAS} - V_{FB}) / R3) - (V_{FB} / R4) - I_{FB}$$

$$I_{LED} = (V_{FB} - R2 \times (((V_{BIAS} - V_{FB}) / R3) - (V_{FB} / R4) - I_{FB})) / R1$$

I_{LED} should be the design full current.

When PWM dimming signal is high (almost equal to V_{PWM_H}):

$$I_{LED} = V_{R1} / R1$$

$$V_{R1} = V_{FB} - V_{R2}$$

$$V_{R2} = I_{R2} \times R2$$

$$I_{R2} = I_{R3} - I_{R4} - I_{FB} = (V_{R3} / R3) - (V_{R4} / R4) - I_{FB} = ((V_{BIAS} - V_{FB}) / R3) - ((V_{FB} - V_{PWM_H}) / R4) - I_{FB}$$

$$I_{LED} = (V_{FB} - R2 \times (((V_{BIAS} - V_{FB}) / R3) - ((V_{FB} - V_{PWM_H}) / R4) - I_{FB})) / R1$$

I_{LED} should be a little negative current to make sure that LED is full dark.

In this demo board, GMT choose $R1 = 27\Omega$, $R2 = 120\text{K}\Omega$, $R3 = 240\text{K}\Omega$, $R4 = 620\text{K}\Omega$.

When PWM signal is low:

$$I_{LED} = (1.2\text{V} - 120\text{K}\Omega \times (((3\text{V} - 1.2\text{V}) / 240\text{K}\Omega) - (1.2\text{V} / 620\text{K}\Omega) - 30\text{nA})) / 27\Omega = 19.7\text{mA}$$

When PWM signal is high:

$$I_{LED} = (1.2\text{V} - 120\text{K}\Omega \times (((3\text{V} - 1.2\text{V}) / 240\text{K}\Omega) - ((1.2\text{V} - 3\text{V}) / 620\text{K}\Omega) - 30\text{nA})) / 27\Omega = -1.79\text{mA}$$

U2: G914C is a micro power LDO regulator that make by GMT. It could regulate a +3VDC from a +3V ~ +5.5V power source. The +3VDC provide as V_{BIAS} for PWM dimming bias voltage, and provide as the power of U3.

U3: PIC12C509A is a 8bit micro controller that make by Microship. It is programmed as a PWM dimming signal generator, and monitor 3 push button to change PWM duty and frequency for dimming control.

Note: You need download the hex code to program a blank new PIC12C509A before solder it on demo board. You could download this hex code from GMT web site <http://www.gmt.com.tw>

